

# Asynchronous Sequential Circuit

# Introduction

- Asynchronous sequential circuit, also called Event Driven Circuit does not have any clock to trigger change of state.
- States changes are triggered by change in input signal i.e. the Circuit behavior is determined by signals at any instant in time and the order in which input signals change.

### **Where we use Asynchronous sequential circuits??**

- These are used when speed of operation is important. As they are independent of internal clock pulse, they operate quickly. so they are used in Quick response circuits.
- Used in the communication between two units having their own independent clocks.
- Used when we require the better external input handling.


### **DRAWBACKS:**

- Asynchronous sequential circuits are more difficult to design.
- Though they have a faster performance, their output is uncertain


# Analysis of Asynchronous Sequential Circuit
 
## AND Gate

- The two input AND gate with output feedback as one input is shown figure (a).
- The circuit is redrawn as shown in figure (b) that includes the effect of propagation delay of the gate say ( $\tau$ ), the finite time after which gate reacts to input.
- Thus, if  $X$  is current output obtained following logic relation and  $x$  is the feedback output we write,  $x = X(t - \tau)$ .
- In the given truth table (state table), encircled state indicate stable conditions of the circuit.



(a) AND gate

 

(b) AND gate with propagation delay

$x \backslash A$	0	1
0	①	①
1	0	①

$$X = x.A$$

(c) Truth table

- For any state, if  $x=X$  then the circuit is stable and if  $x \neq X$ , it is unstable

# NAND Gate

- For  $A=1$  there is no stable state and  $x=X'$  for both  $x=0$  and  $x=1$ . Thus there is oscillation between  $x=0$  and  $A=1$  and  $x=1$  and  $A=1$  state.


 


Figure: Two input NAND gate with output feedback
 
# Two Input NAND Latch

- Constraint to be followed in asynchronous circuit:
- Though there can be more than one input feeding the circuit, *at a time only one input variable can change*. The other input can change only when the circuit is stabilized following the previous input change. The time required the circuit is in the order of propagation delay of gate i.e. in nanosecond order.
- Similarly, if there are two or more output variables *only one output variable can change at any time instant*, as propagation delays in different paths are different.



(b) Truth table

		AB			
		00	01	11	10
x	0	1	①	①	1
	1	①	0	①	①

- for any given combination of x, a, B if  $X=x$ , the circuit is stable otherwise not. Stable states are encircled and arrows show the movements from the transient states,

**Figure:** Two input NAND Latch

For each input combination the circuit has at least one stable state and this stable state will be the starting point of our discussion in each case.


- **Input AB change from 00 to 01:** The circuit move from  $x_{AB}=100$ , a stable position to  $x_{AB}=101$  which is unstable then moves to  $x_{AB}=001$ , a stable state that has output 0. therefore, a  $00 \rightarrow 01$  transition in AB has output X making  $1 \rightarrow 0$  transitions.
- **Input AB changes from 00 to 10:** the circuit from  $x_{AB}=100$ , a stable position to  $x_{AB}=110$ , another stable state has output 1. therefore, a  $00 \rightarrow 10$  transition in AB does not alter the value of output  $X=1$ .
- Note that AB cannot change from 00 to 11 as there will be finite delay. Thus, the transition path of AB is either  $00 \rightarrow 01 \rightarrow 11$  ( then output changes as  $1 \rightarrow 0 \rightarrow 0$ ) or  $00 \rightarrow 10 \rightarrow 11$  ( output changes as  $1 \rightarrow 1 \rightarrow 1$ ) depending upon on which A or B changes earlier. Therefore, output is 0 or 1 depending upon intermediate value and in asynchronous design such transitions are not allowed.



# Transition Table of NAND Latch


<i>Input AB</i>	<i>State(xAB) transition</i>	<i>Output X</i>	<i>Remark</i>
00→01	100→101→001	1→0→0	At $AB = 00$ , stable $x = 1$ ,
00→10	100→110	1→1	
01→00	001→000→100	0→1→1	At $AB = 01$ , stable $x = 0$ ,
01→11	001→011	0→0	
10→00	110→100,	1→1	At $AB = 10$ , stable $x = 1$ ,
10→11	110→111	1→1	
11→01	011→001, 111→101→001	0→0, 1→0→0	At $AB = 11$ , stable $x = 0, 1$ .
11→10	011→010→101, 111→110	0→1→1, 1→1	

# Analyze the given Mealy Model asynchronous sequential circuit

 

**Figure:** An asynchronous sequential circuit: Mealy model

 - Consider  $x = X(t - \tau)$  where  $\tau$  is the cumulative propagation delay from input side up to X.
- Stable states are encircled when  $X = x$ .
- Two stable states  $x = 0$  and  $x = 1$ .
- For all possible combination of  $xAB$  we get X and Y following logic relation shown in the circuit.
- Prepare k-map and state diagram.




a) Karnaugh map, b) state diagram for asynchronous circuit given
 
# Problems with Asynchronous Sequential Circuits

- Oscillation
- Critical race
- Hazards

- Consider an asynchronous sequential circuit with two inputs A and B and two outputs, X and Y.
- Both the outputs are fed back to the input side in the form of x and y but with different propagation delays. Thus x and y cannot change simultaneously but with time delays  $\tau_1$  and  $\tau_2$  respectively and we can write  $x=X(t-\tau_1)$  and  $y=Y(t-\tau_2)$ .
- The stable states are encircled in the circuit where  $xy=XY$ . But there are certain major problems with this truth table.



(a) Block diagram

AB		00	01	11	10
xy	00	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11
	01	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11
	11	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11
	10	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11	⓪⓪ → 11

Critical race      Noncritical race

(b) Truth table

**Figure:** Block diagram and truth table of 2 input , 2 outputs asynchronous circuit

# Oscillation

- Consider, the stable state  $xyAB=0000$ , where  $x=X$  and  $y=Y$ . if the input  $AB$  changes from  $00$  to  $10$ , the circuit goes to  $xyAB=0010$  state and then output  $XY=01$ . This is transient because  $xy \neq XY$ . After time  $\tau_2$ ,  $y$  take the value of  $Y=1$  and the circuit goes to  $xyAB=0110$  where output  $XY=00$ . This again is transient state and after another propagation delay of  $\tau_2$ , the circuit goes through  $xyAB=0010$ . thus the circuit oscillates between state  $0010$  and  $0110$  and the output  $Y$  oscillates between  $0$  and  $1$  with time gap  $\tau_2$ . In asynchronous sequential circuits for any given input, transitions between two unstable states like these are to be avoided to remove oscillation.

# Critical Race

- This occurs when an input change tries to modify more than one output.
- Consider stable state  $xyAB=0000$ . Now, if  $AB$  changes to  $01$  the circuit moves to  $xyAB=0001$  where  $XY=11$ . Now depending which of  $\tau_1$  and  $\tau_2$  is lower,  $xy$  moves from  $00$  to either  $01$  and  $10$ .
- If  $\tau_1$  is lower,  $x$  changes earlier and the circuit goes to  $xyAB=1001$  which is a unstable state with output  $XY=11$ . the circuit next moves to state  $xyAB=1101$  which is a stable state and final output is  $XY=11$ .
- If  $\tau_2$  is lower,  $y$  changes earlier and the circuit goes to  $xyAB=010$ , a stable state and final output is  $01$ .
- Thus, depending upon on propagation delays in feedback path, **the circuit settles at two different states generating two different set of outputs**. Such a situation is called critical race condition and is to be avoided in asynchronous sequential circuit.

- Race can be non-critical too, in which case its presence does not pose any problem for the circuit behavior.
- Consider stable state  $xyAB=1110$ . if the input  $AB$  changes to  $11$ , the circuit goes to  $xyAB=1111$  where output  $XY=00$ .
- Again depending of propagation delays  $xy$  becomes either  $01$  and  $10$ . if  $xy=01$ , then the circuit moves to  $xyAB=0111$  and then to  $0011$  and settles there. If  $xy=10$  then the transition path is  $1111 \rightarrow 1011 \rightarrow 0011$ .
- In both cases final state is  $0011$  and output is  $00$ .
- Since, the race condition does not lead to two different state it is termed as non-critical race.

# Hazards

- Static and dynamic hazards causes malfunctioning of asynchronous sequential circuit.
- Situations like  $Y=A+A'$  and  $Y=AA'$  are to be avoided for any input output combination with the help of hazards covers in truth table.
- Other problem → essential hazards → occurs when change in input does not reach one part of the circuit while from other part one output fed back to the input side becomes available → avoided by adding delay, by adding gates that does not change the logic level, in the feedback path.



# Design of asynchronous sequential circuit

## The problem:

- A digital logic circuit is to be designed that has two inputs A, B and one output X. X goes high if at A=1, B makes a transitions  $1 \rightarrow 0$ . X remains high as long as this A=1, B=0 are maintained. If any of A or B changes at this time output X goes low. It becomes high again when at A=1, B goes from 1 to 0.
- Solution

 


Figure: State diagram of the problem using Moore model

- Primitive table or primitive flow table or flow table

	AB				
	00	01	11	10	X
a	(a)	b	×1	c	0
b	a	(b)	d	×2	0
c	a	×3	d	(c)	0
d	×4	b	(d)	e	0
e	a	×5	d	(e)	1


State Reduction using  
implicant table

b	d,×1 c,×2			
c	d,×1 b,×3	b,×3 c,×2		
d	d,×1 c,e	a,×4 e,×2	a,×4 b,×3 c,e	
e				
	a	b	c	d

Reduced state table  
and state transition  
diagram

	AB				
	00	01	11	10	X
a	(a)	(a)	d	(a)	0
d	×4	a	(d)	e	0
e	a	×5	d	(e)	1


(a)

 

## State assignment

- a:00
- d:01
- e:11
- $\emptyset$  : 10  $\rightarrow$  dummy state

Modified state transition diagram

 

$AB$	00	01	11	10
$pq$				
00	00	00	01	00
01	×	00	01	11
11	10	×	01	11
10	00	×	×	×

(a)

$AB$	00	01	11	10
$pq$				
00	0	0	1	0
01	×	0	1	1
11	0	×	1	1
10	0	×	×	×

$$Q = qA + AB$$

(c)

$AB$	00	01	11	10
$pq$				
00	0	0	0	0
01	×	0	0	1
11	1	×	0	1
10	0	×	×	×

$$P = q\bar{B}$$

(b)

$Q$	0	1
$P$		
0	0	0
1	0	1

$$X = PQ$$

(d)

a) Reduced state diagram b) to d) k-map and design equations

- We represent state variable by P and Q, the corresponding feedback variables are represented by p and q respectively.
- We use Karnaugh map to get expression of state variables P and Q as a function of input A, B and feedback variables p and q.
- The equation of output is generated from P and Q

 


Figure: Circuit diagram of given problem