

# Digital Integrated Circuit

Unit-9

# Transistor Transistor Logic (TTL)

- Introduced in 1964 by Texas Instruments
- Widely used family of digital devices.
- Fast, inexpensive, and easy to use.
- Uses active-low and active high signals
- Types:
  - Standard
  - High-speed
  - Low power
  - Schottky, and
  - Low-power Schottky
- Open collector and tristate devices → backbone of modern computer and digital systems; used to build buses
- Other digital family mostly used in CMOS → has very low power dissipation, so used in battery-powered equipment such as pocket calculators, digital wristwatches, and portable computers.

# Switching Circuits

- Semiconductor devices used in digital integrated circuits include
  - diodes
  - bipolar junction transistors (BJTs), and
  - metal-oxide semiconductor field-effect transistor (MOSFETs)
- Mostly used TTL families : 7400 and 74LS00
- Mostly used CMOS families: 74C00 and 74HC00
- Basic elements used to construct these circuits are:
  - resistors
  - diodes, and
  - BJTs

# The Semi conductor Diode

- Semi conductor diode sometimes called a *pn* junction
- Behaves like a one-way switch.

 


Figure: Semiconductor Diode

- When forward-biased, the diode conducts current, and the voltage across the diode terminals is about  $0.7\text{V}$ .
- When reverse biased, the diode will not conduct current; the diode will act like an open switch. The voltage across the diode terminal depends on the external circuits.


Q. For each diode in figure, determine whether the diode is forward or reverse biased. Determine the diode current  $I$  in each case.

*Solution*

- (a) The current direction is from +5 Vdc to ground, and thus the diode is forward-biased. The voltage across the diode terminals is 0.7 Vdc, and the diode current is found as

$$I = (5 - 0.7)/1 \text{ k}\Omega = 4.3/1 \text{ k}\Omega = 4.3 \text{ mA}$$

 
- (b) The current direction is from +12 Vdc to ground, thus the diode is reverse-biased. The diode current is then  $I = 0.0 \text{ mA}$ . There is no voltage across the 10-k $\Omega$  resistor, and thus the voltage across the diode terminals is 12 Vdc.



Figure

# LEDs


- LED = light emitting diode
- The arrows indicate light emission capability.
- When forward biased, it emits light in the visible spectrum and is thus used as an indicator.
- The voltage across the diode terminals when forward biased is greater than 0.7V.  $V_f$  varies with color of the emitted light.
- The color of the emitted light depends on the element added to the semiconductor material during manufacturing.

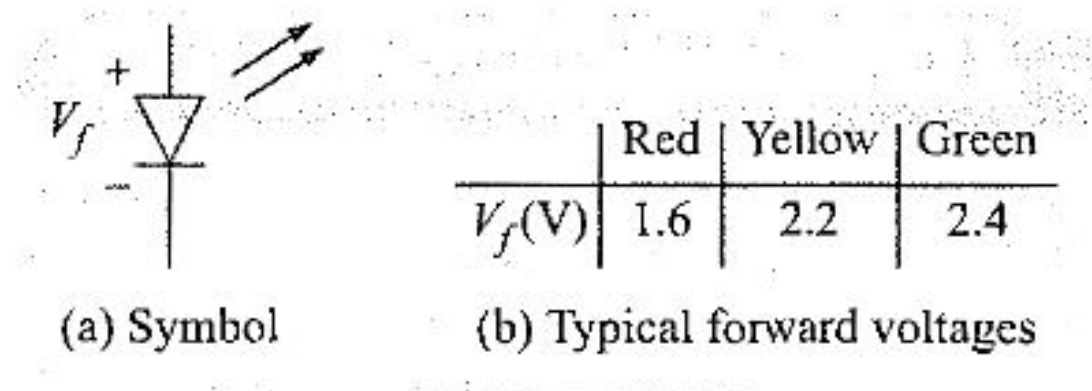


**Figure:** LED symbol and forward biased voltage for different color
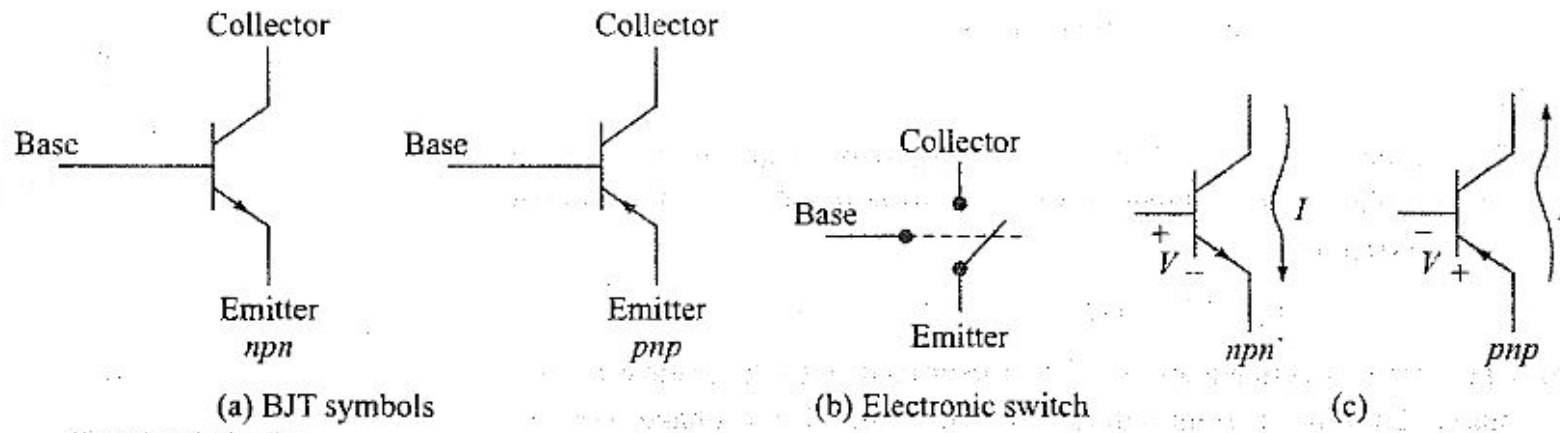
# Bipolar Junction Transistor (BJT)

- Available in two polarities: npn and pnp.
- BJT terminals: collector, emitter and base.
- BJT behaves as switch, by applying a voltage between base and emitter.
- When  $V_{BE}=0$ , the switch is off  $\rightarrow$  no current between Collector and emitter; the transistor is off.
- When  $V_{BE}=V$  volt, the switch is ON  $\rightarrow$  current between Collector and emitter; the transistor is ON. The voltage between emitter and collector ( across a closed switch) is zero!
- For the npn, the base must be more positive than the emitter. The opposite is true for pnp.



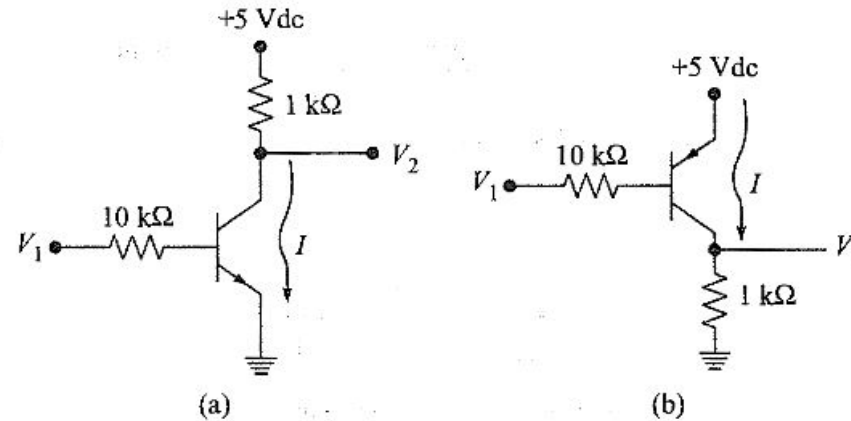Q. Determine the current  $I$  and the voltage  $V_2$  for the circuit given below if i)  $V_1 = 0$  Vdc and ii)  $V_1 = +5$  Vdc




### Solution

- $V_1 = 0$  Vdc. There is no current in the 10-k $\Omega$  resistor. Thus the voltage base-emitter is zero. The BJT is off (switch is open). The BJT current and the current in the 1-k $\Omega$  resistor is zero. The voltage  $V_2$  is +5 Vdc.  
 $V_1 = +5$  Vdc. The base is more positive than the emitter—the BJT is on (switch is closed).  $V_2$  is zero. The BJT current is  $I = 5$  mA.
- $V_1$  is 0 Vdc. The base is more negative than the emitter—the BJT is on (switch closed),  $V_2$  is +5 Vdc. The BJT current is  $I = 5$  mA.  
 $V_1$  is +5 Vdc. There is no current in the 10-k $\Omega$  resistor. The base is at +5 Vdc, and so is the emitter. Thus the voltage base-emitter is zero, and the BJT is off (switch open). The current  $I = 0$  mA, and  $V_2 = 0$  Vdc.



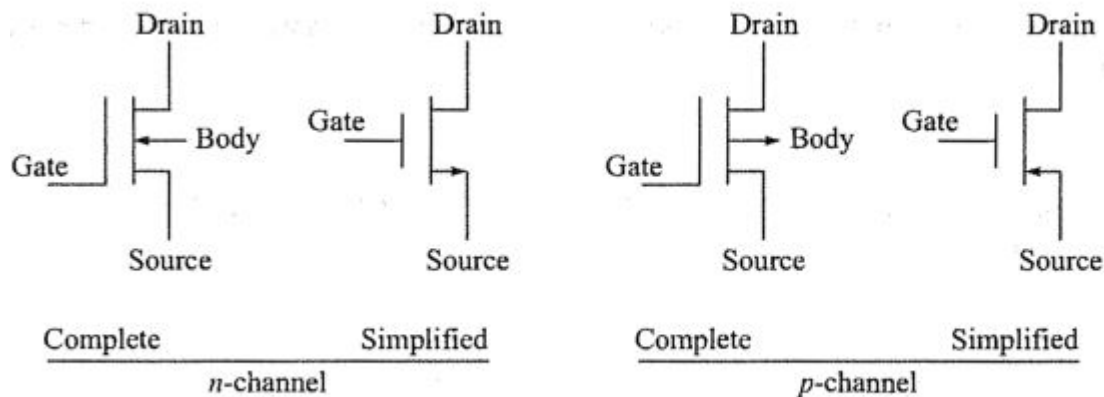
# MOSFETs


- Available in two polarities: n-channel and p-channel
- Operate in “depletion” or “enhancement” mode devices.
- MOSFETs terminals: *gate, source and drain*.
- Behaves as switch, by applying a voltage between gate and source.
  - When  $V_{GS}=0$ , the switch is open; no current is allowed between source and drain; the transistor is off.
  - When  $V_{GS}=V$  volt, the switch is closed; current is allowed between source and drain; the transistor is on. The voltage between source and drain ( across a closed switch) is zero!.
- For the n-channel transistor, the gate must be more positive than the source. The opposite is true for the p-channel transistor.



(a) MOSFET symbols

 


(b) Electronic switch

 

(c)

# Complementary Metal-Oxide-Semiconductor (CMOS) FETs

- NMOS ICs → ICs constructed entirely with n-channel MOSFETs.
- PMOS ICs → ICs constructed entirely with p-channel MOSFETs.
- CMOS ICs → IC constructed using both n-channel and p-channel; n-channel and p-channel MOSFETs are complementary devices. Examples: 74C00 and 74HC00 families.
- A CMOS is an inverter
  - $V_1 = 0$  Vdc,  $Q_n$  is off and  $Q_p$  is on.  $V_2 = +5$  Vdc.
  - $V_1 = +5$  Vdc,  $Q_n$  is on and  $Q_p$  is off.  $V_2 = 0$  Vdc.
- In steady state (while not switching), one of the transistors is always off. So, current  $I = 0$  mA.
- When switching between states, both transistors are on for a very short time because of the rise or fall time of  $V_1$ . this is the only time when current is non zero.
- CMOS is used in application where dc power supply current must be held to a minimum-watches, pocket calculators, etc.
- If the input  $V_1 = +5$  Vdc/2=2.5 Vdc, direct short occurs between + 5 Vdc and ground.

 


**Figure:** CMOS Inverter

# 7400 TTL

## Standard TTL

- Figure: TTL NAND gate
- The multiple emitter input transistors is typical of gates and other devices in the 7400 series.
- Each emitter acts like a diode, therefore,  $Q_1$  and the 4-K $\Omega$  act like a 2-input AND gate. The rest of the circuit inverts the signal so that the overall circuit acts like a 2-input NAND gate.
- The output of transistor ( $Q_3$  and  $Q_4$ ) form totem-pole connection (one npn in series with another).
  - With it, either the upper or lower transistor is on.
  - When  $Q_3$  is on, the output is high; when  $Q_4$  is on, the output is low.

 


**Figure:** Two input TTL NAND gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

**Figure:** Truth Table

- If A or B are low, the base of  $Q_1$  is pulled down to approximately 0.7 V. this reduces the base voltage of  $Q_2$  to almost zero. Therefore,  $Q_2$  cuts off. With  $Q_2$  open,  $Q_4$  is off, and the  $Q_3$  base is pulled high. The emitter of  $Q_3$  is only 0.7 V below the base, and thus the Y output is pulled up to a high voltage.
- When A and B are both high voltages, the emitter diode of  $Q_1$  stops conducting, and the collector diode goes into forward conduction. This forces  $Q_2$  to turn on. In turn,  $Q_4$  goes on and  $Q_3$  turns off, producing a low output.
- Without diode in  $D_1$  in the circuit,  $Q_3$  will conduct slightly when the output is low. To prevent this, the diode is inserted; its voltage drop keeps the base-emitter diode of  $Q_3$  reverse biased. In this way, only  $Q_4$  conducts when the output is low.

 

**Figure:** Two input TTL NAND gate

## **Propagation delay time**

- The time it takes for the output of a gate to change after the inputs have changed.
- The propagation delay time of TTL gate is approximately 10 ns.

## **Power dissipation**

- A standard TTL gate has power dissipation of about 10 milliwatt (mW).
- It may vary from this value because of signal levels, tolerances etc. but on average it is 10 mW.

# Device Number

Device Number	Description
7400	Quad 2-input NAND gates
7402	Quad 2-input NOR gates
7404	Hex Inverter
7408	Quad 2-input AND gates
7410	Triple 3-input NAND gates
7411	Triple 3-input AND gates
7420	Dual 4-input NAND gates
7421	Dual 4-input AND gates
7425	Dual 4 input NOR gates
7427	Triple 3-input NOR gates
7430	8-input NAND gate
7486	Quad 2-input XOR gates

# 5400 Series

## **7400 series**

- Temperature range of 0 to 70°C
- Supply range: 4.754 to 5.25 V.
- Adequate for commercial application

## **5400 series**

- Temperature range: -55 to 125°C
- Supply range: 4.5 to 5.5 V
- Developed for military applications
- Rarely used for commercial because of high cost

# High speed TTL

- By decreasing the resistance a manufacture can lower the time the internal time constants; this decreases the propagation delay time.
- Smaller resistance however increases power dissipation.
- This design variation is known as high speed TTL.
- Device number: 74H00, 74H02, so on.
- Power dissipation: approximately 22mw
- Propagation delay: approximately 6ns




# Low-Power TTL

- By increasing the internal resistance a manufacture can reduce the power dissipation of TTL gates. This design variation is known as low-power TTL.
- Device are numbers 74L00, 74L02 and so on.
- This devices are slow because of large internal time constants and has propagation delay time of bout 35 ns.
- Has power dissipation of bout 1 mW.

# Schottky TTL

- Problem with standard TTL, high-speed TTL and low-power TTL → saturation delay time.
  - In these types, the transistor are switched with on with excessive current, causing a surplus of carriers to be stored in the base. When you have to switch a transistor from on to off, you have to wait for the extra carriers to flow out of the base. This delay is referred as saturation delay time.
- Schottky TTL reduces saturation delay time.
- Has forward voltage of 0.25 to 0.4 V → prevents saturation from saturating fully. This virtually eliminates saturation delay time, which means better switching speed.
- Devices are numbers as 74S00, 74S02, and so on.

 

**Figure:** Schottky Diode

# Low-Power Schottky TTL


- By increasing internal resistance and using Schottky diode, there comes a compromise between low power and high speed:  
Low-power Schottky diode.
- Devices are numbered as 74SL00, 74SL02, so on.
- Power dissipation: around 2 mW
- Propagation delay time: around 10 ns.

# TTL Parameters

- Floating Inputs
- Worst-Case Input voltages
- Worst-Case Output voltages
- Profiles and Windows
- Sourcing and Sinking
- Noise Immunity
- Standard Loading

# Floating Inputs

- When TTL input is high, the emitter current is nearly zero. (fig. a)
- When TTL input is *floating* (unconnected, fig. b), no emitter current is possible because of the open circuit. Therefore, a floating TTL input is equivalent to a high output.

 

**Figure:** a) High input, b) Open is equivalent to high input, c) Direct connection to supply voltage, d) High input through a pull-up resistor

# Worst-Case Input Voltages

- Figure shows a TTL inverter with an input voltage of  $V_i$  and an output voltage of  $V_o$ .
- When  $V_i = 0$  V, it is in low state and designated as  $V_{IL}$ . It can range from 0 V to 0.8 V. So, worst case low input  $V_{IL, \max} = 0.8$  V.
- If  $V_i > V_{IL, \max}$ , the output state is unpredictable.
- High state input voltage,  $V_{IH}$  ranges from 2 to 5 V. So, worst case high input  $V_{IH, \min} = 2$  V.
- When  $V_i < V_{IH, \min}$ , the output state is unpredictable.

 


Figure: a) TTL inverter b) TTL Input Profile c) TTL output profile

# Worst Case Output voltage

- Ideally, the low output state is 0 V and the high output state is 5 V. because of internal voltage drop inside TTL devices, we cannot achieve these values.
- When the output voltage is low,  $Q_4$  is saturated and has a small voltage drop across it. With TTL devices, any output voltage from 0 to 0.4 V is considered as a low output and designated as  $V_{OL}$ .
- When the output is high,  $Q_3$  acts as emitter follower. Because of the voltage drop across  $Q_3$ , D1, and 130 $\Omega$  resistor, the output voltage will be less than supply voltage. With TTL devices, the high-state output voltage is designated  $V_{OH}$  and has a value between 2.4 to 3.9 V. so  $V_{OH}$ , worst case high output min=2.4 V
- Any output between 0.4 and 2.4 V is indeterminate under worst-case conditions.

# Profile and windows

- The input characteristic of figure a and output characteristic of figure b are called TTL input profile and TTL output profile respectively. Each rectangular area in figure can be thought as window.
- There is a low window(0 to 0.8V), an indeterminate window (0.8 to 2.0 V), and high window (2.0 to 5.0 V) in input profile. Similar in output profile.

## Values to Remember (worst case values)

- $V_{IL, \max} = 0.8 \text{ V}$
- $V_{IH, \min} = 2 \text{ V}$
- $V_{OL, \max} = 0.4 \text{ V}$
- $V_{OH, \min} = 2.4 \text{ V}$


 


Figure: a) TTL Input Profile

 

b) TTL Output Profile




# Compatibility

- TTL devices are compatible because the low and high output window fit inside the low and high input windows.
- Therefore, the output of any TTL devices is suitable for driving the input of another TTL devices.
- Figure below shows one TTL device driving another. The first device is called a *driver* and the second is a *load*.






(a)

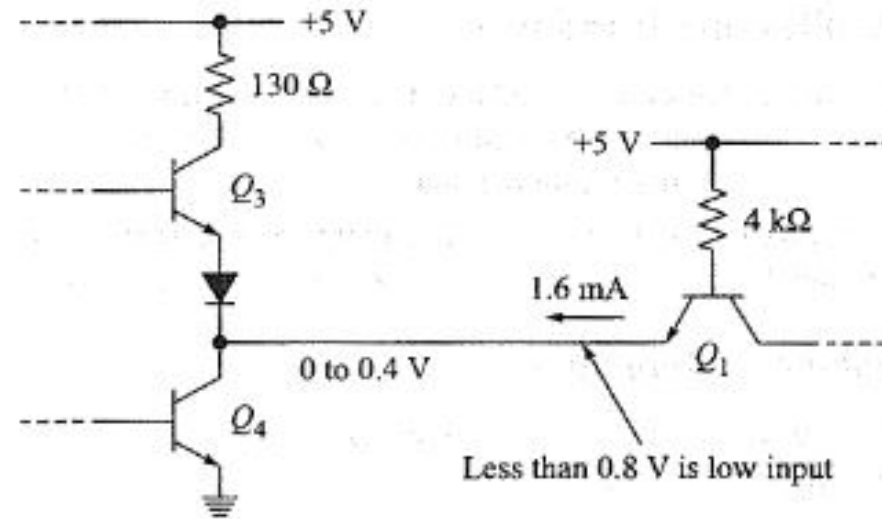

(b)

 - When standard TTL output is low, an emitter current of around 1.6 mA exits in the direction shown.
- Because it is saturated,  $Q_4$  acts like **current sink**.



(c)

- When the standard TTL output is high, a reverse emitter current of 40  $\mu\text{A}$  exits in the direction shown.
- $Q_3$  is acting **as current source**.

### Worst case input currents



$$I_{I,\max} = -1.6 \text{ mA} \quad I_{LH,\max} = 40 \text{ } \mu\text{A}$$


**Figure:** Sinking and sourcing current

# Noise Immunity

- In worst case, there is a difference of 0.4 V between the driver output voltages and required load input voltage. For instance, the worst case values are:
  - $V_{OL, \max} = 0.4 \text{ V}$
  - $V_{IL, \max} = 0.8 \text{ V}$
- Similarly, the worst case high values are
  - $V_{OH, \min} = 2.4 \text{ V}$
  - $V_{IH, \max} = 2 \text{ V}$
- In either case, the difference is 0.4 V. This difference is called noise *immunity*. It represents built in protection against noise.

# Why do we need protection against noise?

- The connecting wires between a TTL driver and load is equivalent to a small antenna that picks up stray noise signals.
- In worst case
- $V_{IL} = V_{OL} + V_{noise} = 0.4 \text{ V} + V_{noise}$
- $V_{IH} = V_{OH} - V_{noise} = 2.4 \text{ V} - V_{noise}$
- The TTL load has an input that is on the verge of being unpredictable in a noisy environment. The slightly additional noise voltage may produce a false change in the output state of the TTL load.

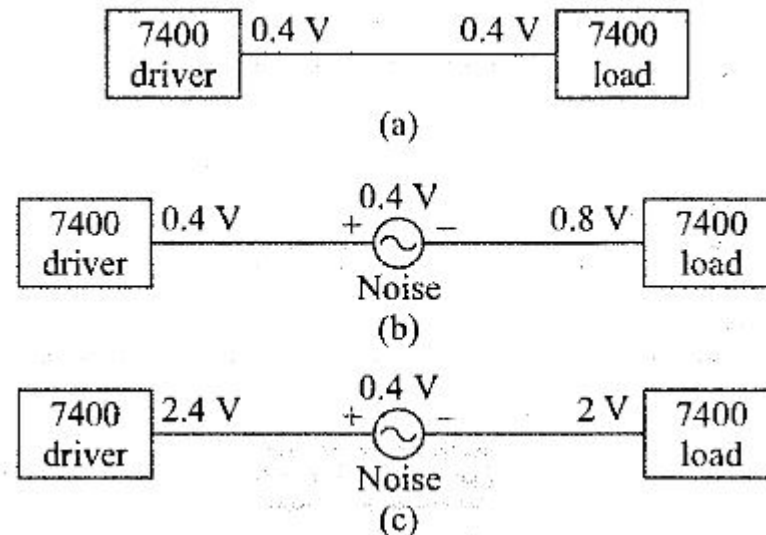

**Figure:** a) TTL driver and load      b) False triggering into high state,      c) False Triggering into low state

# Standard Loading

- A TTL device can source current ( high output) or sink current (low output).
- $I_{OL, \max} = 16 \text{ mA}$
- $I_{OH, \max} = -400 \text{ } \mu\text{A}$
- $I_{IL, \max} = -1.6 \text{ mA}$
- $I_{IH, \max} = 40 \text{ } \mu\text{A}$
- Since, the maximum output currents are 10 times larger than the input currents, we can connect up to 10 TTL emitters to any TTL output.

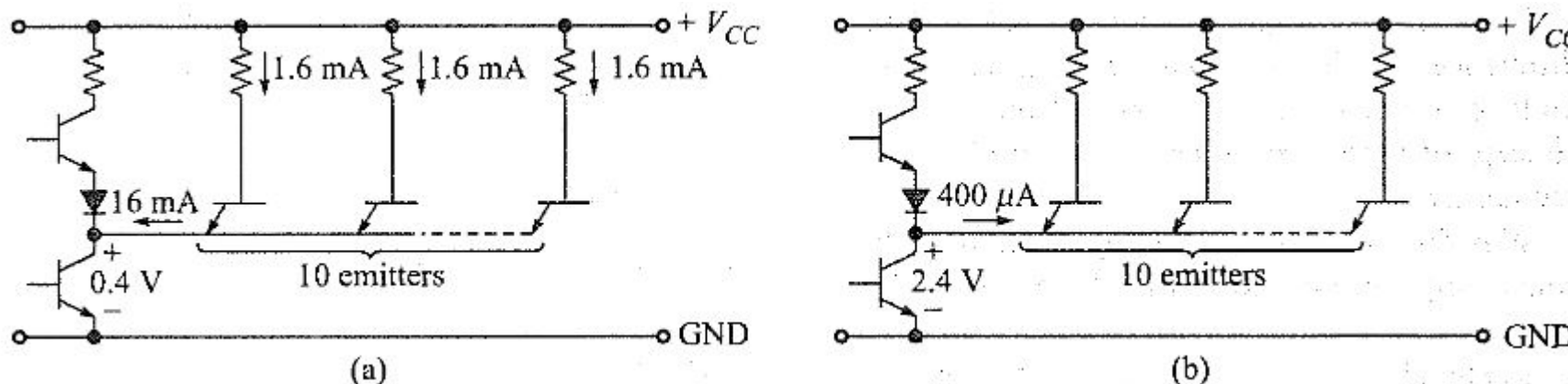


Figure: a) Low-state fanout b) High-state fanout

Fan-out is a term that defines the maximum number of digital inputs that the output of a single logic gate can feed. Fan-in is a term that defines the maximum number of digital inputs that a single logic gate can accept

<i>TTL Driver</i>	<i>TTL Load</i>				
	<i>74</i>	<i>74H</i>	<i>74L</i>	<i>74S</i>	<i>74LS</i>
74	10	8	40	8	20
74H	12	10	50	10	25
74L	2	1	20	1	10
74S	12	10	100	10	50
74LS	5	4	40	4	20

**Table:** Fanouts

# TTL Overview

## NAND Gates

- The backbone of the 7400 series.
- All devices in this series are derived from the 2-input NAND gate.
- To produce 3-, 4-, and 8- input NAND gates, the manufacture uses 3-, 4-, and 8- emitter transistors.
- Least expensive devices in 7400 series

## NOR Gates

- Here, Q5 and Q6 have been added to basic NAND gate design.
- Since Q2 and Q6 are in parallel, we get the OR function, which is followed by inversion to get the NOR function.
- When A and B are both low, the bases of Q1 and Q5 are pulled low; this cuts off Q2 and Q6. then Q3 acts as an emitter-follower, and we get a high output.
- If A or B is high, Q1 and Q5 are cut off, forcing Q2 or Q6 turn on. When this happens, Q4 saturates and pulls the output down to a low voltage.
- With more transistors, a manufacture can produce 3- and 4-input NOR gates. (Note: A TTL 8-input NOR gate is not available. )

 


Figure: TTL NOR gate



## **AND and OR gates**

- To produce the AND function, another inverting stage is inserted in the basic NAND gate design. The extra inversion converts the NAND to an AND gate.
- The available NAND gates are: 7408 (quad 2-input), 7411 (triple 3-input), and 7421 ( dual 4-input).
- Similarly, another inverting stage can be inserted in the NOR gate to get OR gate.
- The only available TTL OR gate is the 7432 (quad 2-input).

## Buffer Drivers

- ALL IC buffer can source and sink more current than standard TTL.
- Example: 7347 is a quad 2-input NAND buffer.
- Each gate has following worst case currents:


$$I_{IL} = -1.6 \text{ mA} \quad I_{IH} = 40 \text{ } \mu\text{A}$$

$$I_{OL} = 48 \text{ mA} \quad I_{OH} = -1.2 \text{ mA}$$

- The input currents are the same as those of 7400, but the output current are 3 times as high. That means, it can drive heavier loads. In other words, the fanout of a 7437 is 3 times that of 7400.

# Open-Collector Gates

- Some TTL devices have an *open-collector output*. That is, they use only the lower transistor of a totem-pole pair.

 

**Figure:** Open-collector TTL a) Circuit, b) Pull-up resistor, c) Open-collector outputs connected to a common pull-up resistor

- Because the collector of  $Q_4$  is open, a gate like this will not work properly until you connect an external pull-up resistor.

- The outputs of open-collector gates can be wired together and connected to a common pull-up resistor as in figure c above. (3 TTL devices connected to the pull-up resistor). This is known as *wire-OR* (some called in wire-AND).
- Disadvantages of open-collector gates: slow switching speed → worst when the output goes from low to high.
- Using active pull-up, which uses the modified totem-pole output to speed up the charging of stray output capacitance, switching time can improve.


# Three-state TTL Devices

- Using a common pull-up resistor with open-collector devices is called *passive pull-up* because the supply voltage pulls the output voltage to the high level when all the transistor are cut off.
- *Active pull-up* is the modified form of totem-pole output to overcome the disadvantage of passive pull-up.

## Why standard TTL will not work?

## Low Disable Input

- Three-state totem-pole outputs directly without destroying any devices and, avoids the loss of speed that occurs with open-collector devices.
- When DISABLE is low, the base and collector of  $Q_6$  are pulled low  $\rightarrow$  cuts off  $Q_7$  and  $Q_8$ . therefore, the second emitter of  $Q_1$  and the cathode of  $D_1$  are floating. For this condition, the rest of circuit acts as inverter:
  - a low A input forces  $Q_2$  and  $Q_5$  to cut off, while  $Q_3$  and  $Q_4$  turn on, producing a high output.
  - a high a input forces  $Q_2$  to turn on, which drives  $Q_5$  on and produce a low output.

 


**Figure:** Three-State Inverter

DISABLE	A	Y
0	0	1
0	1	0
1	X	High Impedance

## High DISABLE Input


- When DISABLE is high, the base and collector of  $Q_6$  go high, which turns on  $Q_7$  and  $Q_8$ . Ideally the collector of  $Q_8$  is pulled to ground. This causes the base and collector of  $Q_1$  to go low, cutting  $Q_2$  and  $Q_5$ .
- Also  $Q_3$  is off because of the clamping action of  $D_1$  i.e. the base of  $Q_3$  is only 0.7 V above ground, which is insufficient to turn on  $Q_3$  and  $Q_4$ .
- With both  $Q_4$  and  $Q_5$  off, the y output is floating. Ideally, this means the Thevenin impedance looking back into the Y approaches infinity,

 

**Figure:** Three-state Inverter



# Three-state Buffer

 

**Figure:** Three-state logic diagrams: a) Equivalent circuit of inverter, b) Logic symbol of inverter, c) Logic symbol of buffer


- 74365 is an example of a commercially available three-state hex non-inverting buffer.
- Used in organizing digital components around a bus.

# External Drive for TTL Loads

- To drive a TTL load with an external source, need to satisfy the TTL input requirements for voltage and current.
- For standard TTL,
  - in the low state, an input voltage between 0 and 0.8 v with a current of around 1.6 mA.
  - in the high state, the voltage has to be from 2 to 5 v with current of around 40  $\mu$ A.

# Switch drive


- With switch open, the input is pulled up to +5 V. in worst case, 40  $\mu$ A current exist. So voltage appearing at the input pin,  $V_i = 5 \text{ V} - (40 \text{ } \mu\text{A})(1 \text{ k}\Omega) = 4.96 \text{ V}$ , which is well above minimum requirement of 2 V, which is fine because it means that the noise immunity is excellent.
- When switch is closed, the input is pulled to ground. In worst case, the input current is 1.6 mA. This sink creates no problem because it flows through the closed switch to ground. The noise immunity is fine because the input voltage if 0 V, well below the maximum allowable value of 0.8 V.

 

**Figure:** Switch Drive for TTL Input

# Transistor Drive

- When  $V_i$  is low, the transistor is off and is equivalent to an open switch. Then the TTL input is pulled to +5V through resistance of 1 k $\Omega$ .
- When  $V_i$  is high, the transistor is on and is equivalent to a closed switch. In this case, it easily sinks the 1.6 mA of input current.
- The transistor inverts the control signal  $V_i$ . The double inversion produces an in-phase control signal at the TTL input.

 

**Figure:** a) Transistor drive for TTL input,


b) Inverter eliminates transistor inversion

# TTL Driving External Loads

- Because standard TTL can sink up to 16 mA, TTL driver can be used to control an external load such as relay, LED, etc.
- When the TTL output is high, there is no load current.
- But when the TTL output is low, the lower end of  $R_L$  is ideally grounded. This set up a load current of approximately  $I_L = 5 \text{ V} / R_L$
- Since standard TTL can sink a maximum of 16 mA, the load resistance is limited to a minimum value of about
- $R_L = 5 \text{ V} / 16 \text{ mA} = 312\Omega$ .

## Driving an LED


- When TTL output is high, the LED is off.
- When the TTL output is low, the LED lights up. If the output voltage drop is 2 V, the LED Current is:
- $I_L = (5 \text{ V} - 2\text{V}) / 270\Omega = 11.1 \text{ mA}$ .

 

**Figure:** a) TTL output drives load resistor, b) TTL output drives LED
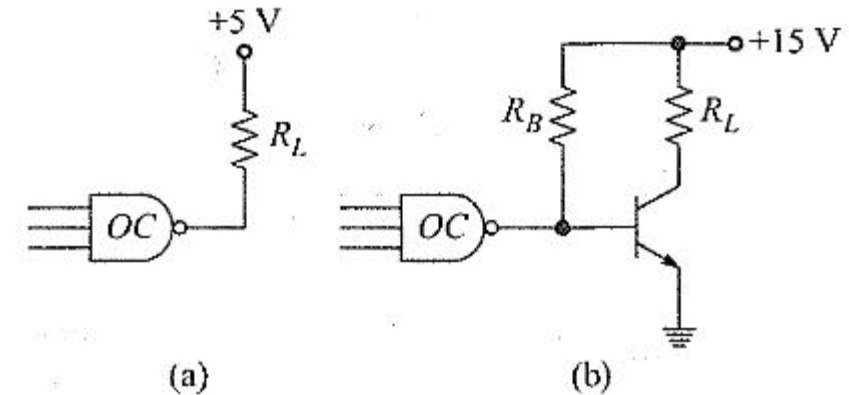
## Supplying Voltage Different from + 5V

- Use open collector TTL Devices
- Since open-collector device can sink a maximum of 16 mA, the minimum load resistance in figure a is 1 k $\Omega$ .
- Use external transistor to get more than 16 mA load current.
- When the open-collector device has a low output, the external transistor goes off and the load current is zero.
- When the open-collector device has a ~~high~~<sup>high</sup> output, the external transistor goes on and the load current is maximum..




# 74C00 Series

- National Semiconductor pioneered the 74C00 series
- Compatible with TTL devices of similar number. For instances, the 74C00 is quad 2-input NAND gates, the 74C02 is quad 2-input NOR gate and so on.
- Contains a variety of small-scale integration (SSI) and medium-scale integration (MSI)
- Useful too build battery-powered equipment

# CMOS NAND Gate

- $Q_1$  and  $Q_2$  form one complementary connection;  $Q_3$  and  $Q_4$  form another.
- A low A will close  $Q_1$  and open  $Q_2$ ; a high A input will open  $Q_1$  and close  $Q_2$ .
- Similarly, a low B input will open  $Q_3$ , and close  $Q_4$ ; a high B input will close  $Q_3$  and open  $Q_4$ .
- The Y output is pulled up to the supply voltage when either  $Q_1$  or  $Q_4$  is conducting.
- The output is pulled to ground only when  $Q_2$  and  $Q_3$  are conducting.

 


**Figure:** A CMOS NAND Gate

A	B	Y
Low	Low	High
Low	High	High
High	Low	High
High	High	Low



- **Case 1:** Here A and B is low. Because A is low,  $Q_1$  is closed. Therefore Y is pulled high through the small resistance of  $Q_1$ .
- **Case 2:** Now A is low and B is high. Since A is still low,  $Q_1$  remains closed and Y stays in the high state.
- **Case 3:** The A input is high and the B is low. Because B is low,  $Q_4$  is closed. This pulls Y up to the supply voltage through the small resistance of  $Q_4$ .
- **Case 4:** The A is high, and the B is high. When both inputs are high,  $Q_2$  and  $Q_3$  are closed, pulling the output to ground.

 

**Figure:** A CMOS NAND Gate

A	B	Y
Low	Low	High
Low	High	High
High	Low	High
High	High	Low

# NOR Gate

- The output goes high only when  $Q_1$  and  $Q_2$  are closed. The output goes low if either  $Q_3$  or  $Q_4$  is closed.

The four possible cases are:

- **Case 1:** The A is low, and the B is low. For both inputs low,  $Q_1$  and  $Q_2$  are closed. Therefore, Y is pulled high through the small resistance of  $Q_1$  and  $Q_2$ .
- **Case 2:** The A is low, and the B is high. Because B is high,  $Q_3$  is closed, pulling the output down to ground.
- **Case 3:** The A is high, and the B is low. With A high,  $Q_4$  is closed. The closed  $Q_4$  pulls the output low.
- **Case 4:** The A is high, and the B is high. Since A is still high,  $Q_4$  is closed and the output remains low.

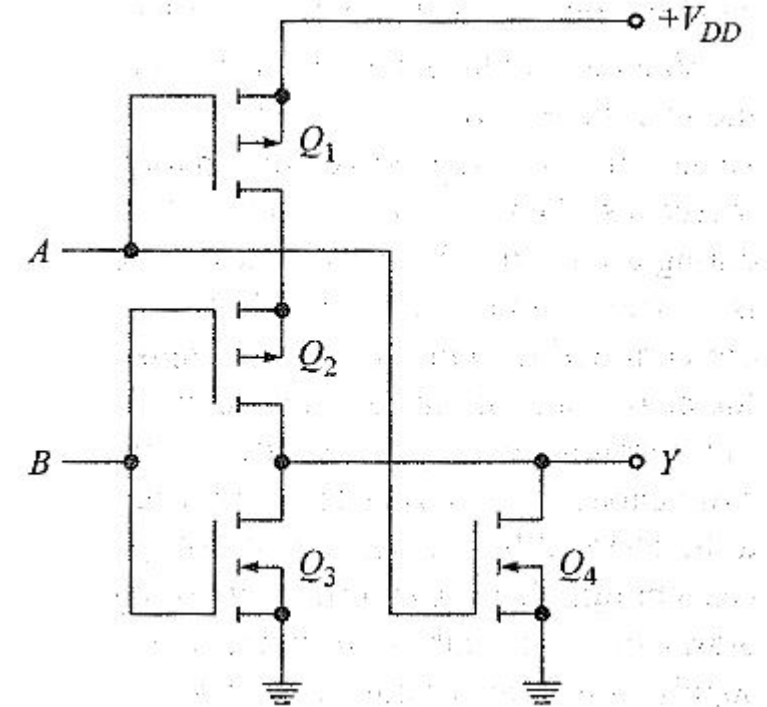


Figure: CMOS NOR Gate

A	B	Y
Low	Low	High
Low	High	Low
High	Low	Low
High	High	Low

# Propagation Delay Time

- Propagation delay time  $t_p$  is approximately 25 to 100ns, with exact value depending upon the power supply voltage and other factors.
- When two or more CMOS gates are cascaded, the propagation delay time of each gates are added together to get total.

# CMOS Characteristics

- 74C00 works over temperature range of -40 to + 85°C and over a supply range of 3 to 15 V.

## Floating Inputs


- Setup a possible noise problem,
- Produce excessive power dissipation
- Because of insulated gates, a floating input allows the gate voltage to drift into the linear region, causing excessive current flow through push-pull stages.

# Easily damaged

- Because of the thin layer of silicon dioxide between the gate and substrate, CMOS devices have a very high input resistance, approximately infinite.
- The insulating layer is kept as thin as possible to give the gate more control over the drain current.
- Because of this layer is so thin, it is easily destroyed by excessive gate voltage.
- One way to protect against overvoltages is to include diodes across the input.

# Transfer Characteristic of a CMOS Inverter


- When the input voltage is low state, the output voltage is in the high state.
- As the input voltage increases, the output remains in the high state until a threshold is reached.
- Somewhere near an input voltage  $V_{CC}/2$ , the voltage greater than  $V_{CC}/2$  holds the output in the low state.
- This transfer characteristic is an improvement over TTL because:
  - The indeterminate region is much smaller
  - Noise immunity <sup>is</sup> 45 percent of  $V_{CC}/2$
  - The logic swing between the low and high output states approximately equals the supply voltage.

 

**Figure:** Transfer Characteristic of a CMOS gate
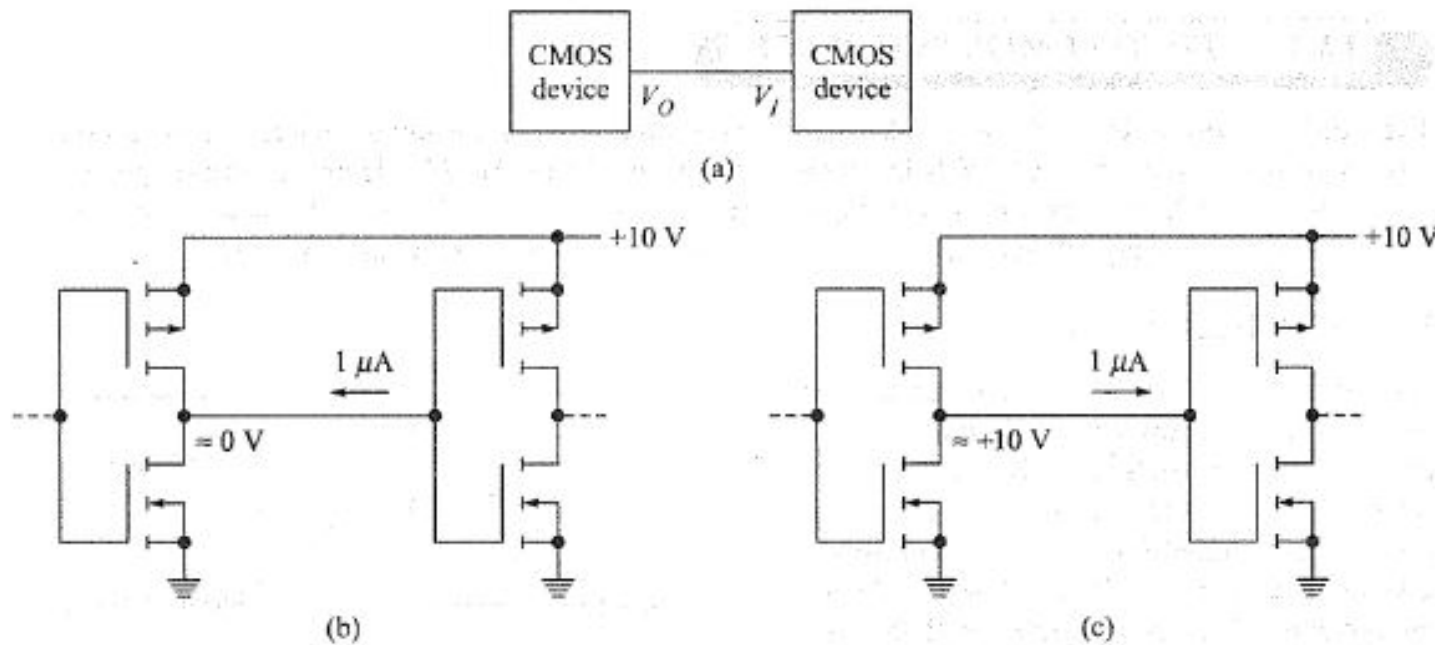
# Compatibility

- CMOS devices are compatible with one another because the output of any CMOS device can be used as the input to another CMOS device.



Worst-case input currents for CMOS devices:

$$I_{IL, \max} = 1 \mu A \quad I_{IH, \max} = 1 \mu A$$

$$I_{OL, \max} = 10 \mu A \quad I_{OH, \max} = -10 \mu A$$



Fanout: 10

**Figure:** a) output of CMOS device drive input of another CMOS device,  
b) Sink current c) source current

# TTL-To-CMOS Interface

- The word interface refers to the way a driving device is connected to a loading device.
- TTL devices need a supply voltage of 5 V, while CMOS devices can use any supply voltage from 3 to 15 V.
- Because the supply requirements differ, several interfacing schemes may be used.



# Interfacing at supply voltage 5 V

- There is no problem with TTL low-state window (0 to 0.4 V) because it fits inside the CMOS low-state window (0 to 1.5 V). This means, the CMOS load always interprets the TTL low-state drive as a low.
- The problem is in the TTL high state. Need to do something extra to make the two different devices compatible. → standard solution is to use a pull up resistor between TTL driver and the CMOS load as shown in figure below.

 


Figure: TTL driver and CMOS load


 



Figure: a) TTL output profile  
b) CMOS input profile

- When TTL output is low, the lower end of the 3.3 k $\Omega$  is grounded. Therefore, the TTL driver sinks a current of roughly  $I = (5 \text{ V}/3.3 \text{ k}\Omega) = 1.52 \text{ mA}$ .
- When TTL output is high, the output voltage is pulled up to +5 V
- In worst case,  $I_{OL, \max} = 16 \text{ mA}$  and supply voltage can be as high as 5.25 V, so minimum resistance is
- $R_{\min} = (5.25 \text{ V}/16 \text{ mA}) = 328\Omega$
- The standard value is 330  $\Omega \rightarrow$  use this if switching speed is critical.
- In many application, a pull-up resistance of 3.3 k $\Omega$  is fine.

 

# Different supply voltage


- CMOS performance deteriorates at lower voltages because the propagation delay time increases and the noise immunity decreases.
- So, CMOS devices is better to run with supply voltage between 9 and 12 V.
- When TTL output is low, the supply voltage is pulled to ground with  $I_{\text{sink}} = (12 \text{ V} / 6.8 \text{ k}\Omega) = 1.76 \text{ mA}$ .
- When TTL output is high, the open-collector rises passively to +12 V; this produces slower switching action than before.
- For instance, with gate capacitance of 10 pF, the pull-up time is  $RC = (6.8 \text{ k}\Omega) (10 \text{ pF}) = 68 \text{ ns}$ .
- If this is a problem , reducing pull up resistor to its minimum allowable value of
$$R_{\text{min}} = (12 \text{ V}) / (16 \text{ mA}) = 750 \text{ ohm}$$
Pull-up time constant decrease to  $RC = (750 \text{ }\Omega) (10 \text{ pF}) = 7.5 \text{ ns}$

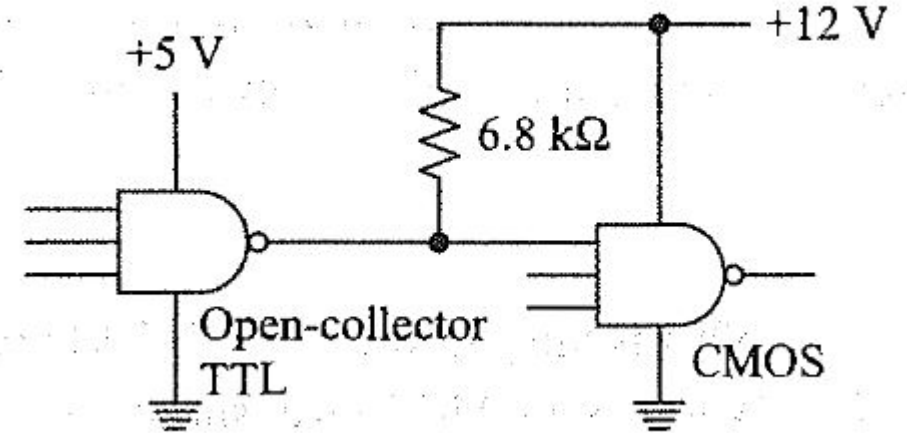

**Figure:** open-collector TTL driver allows higher CMOS supply voltage

# CMOS Level Shifter

- The input stage of the chip uses a supply voltage of +5V, while the output stage uses +12 V. In other words, the input stage interfaces with TTL, and the output stage interfaces with CMOS.
- A standard TTL device drives the level shifter, producing active TTL pull up to at least +2.4 V. the voltage can be pull up beyond this, causing valid high-state input to the level shifter.
- Since, the output of the level shifter connects to +12 V, it has better propagation delay time and noise immunity. Due to this, level shifter is used between TTL driver and CMOS load.

 

**Figure:** CMOS level shifter allows the use of 5-V and 12-V supplies

# CMOS-To-TTL-Interface

- We have to make sure that the CMOS low-state output is always less than 0.8 V, the maximum allowable TTL low-state input voltage.
- Also, the CMOS high-state output must always be greater than 2 V, the minimum allowable TTL high-state input voltage.

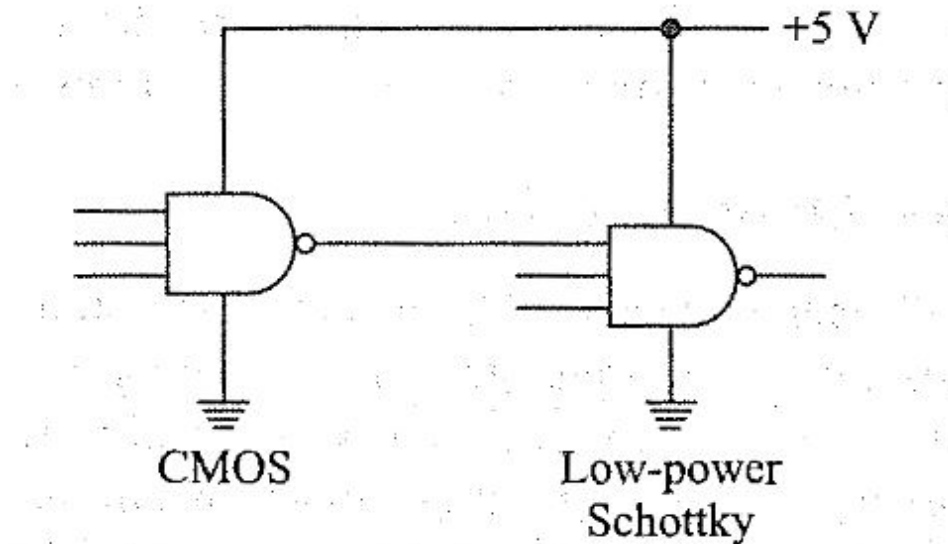


Figure: CMOS driver and low power Schottky TTL Load


 


Figure: a) CMOS input profile b) TTL input profile

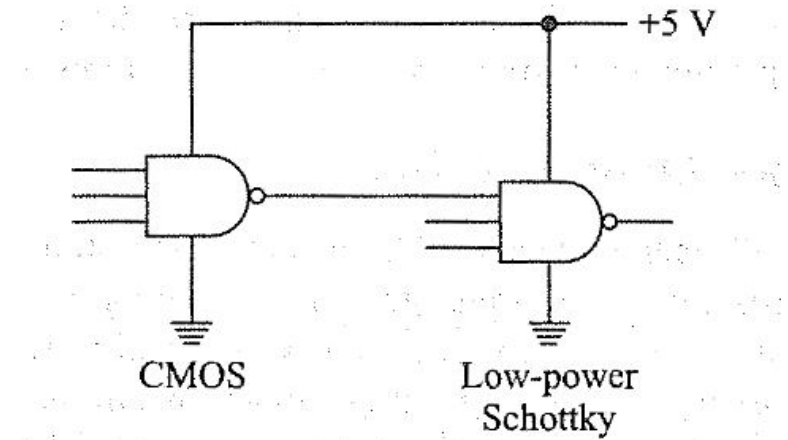
# Supply Voltage at 5 V

- Use +5 V as the supply voltage for the driver and the load
- Low power Schottky device has the worst-case input currents:
- $I_{IL,max} = -360 \mu A$   $I_{IH,max} = 20 \mu A$
- Worst case-output currents for CMOS driving TTL:
- $I_{OL,max} = 360 \mu A$   $I_{OH,max} = -360 \mu A$
- This tells us that a CMOS driver can sink 360  $\mu A$  in the low state, exactly the input current for a low-power Schottky TTL devices. On the other hand, the CMOS driver can source 360  $\mu A$ , which is more than enough to handle the high-state input current (only 20  $\mu A$ ). So the sink current limits the CMOS/TTL fanout to 1.



# Using CMOS Buffer


- The CMOS driver now directly connects to a CMOS buffer, as a chip with larger output currents. For instance, a 74C902 is a hex buffer, or six CMOS buffers in a single package. Each buffer has the worst-case output currents:  $I_{OL,max} = 3.6 \text{ mA}$   $I_{OH,max} = 800 \text{ }\mu\text{A}$
- Since a standard TTL load has a low-state input current of 1.6 mA and a high-state input current of 40  $\mu\text{A}$ , a 74C902 can drive two standard TTL Loads. So the CMOS/TTL fanout is 2

 

**Figure:** CMOS buffer can drive standard TTL load

# Different supply voltage

- CMOS buffer like 74C902 can use a supply voltage of 3 to 15 V and an input voltage of -0.3 to 15 V.
- The input voltage can be greater than the supply voltage without damaging the device. For instance, a high-state input of +12 V can be used even though the supply voltage is only +5 V.

 


**Figure:** CMOS driver runs better with 12-V supply

compiled by: dinesh ghemosu, Khwopa College of Engineering,  
3rd semester, Digital Logic



# Open-Drain Interface

- Open-drain devices have an output stage consisting only of sink MOSFET. 74C906 is a hex open-drain buffer.
- CMOS driver and CMOS buffer run off +12 V, except for the open-drain output which provides the TTL interface.

 

**Figure:** Open-drain CMOS buffer increases sink current.